



Figure 1: ALU Block Diagram

Using the simulation program (Altera Quartus Prime), it is required to make an 4bit ALU unit that able to do the following operations:

Selector “S”	Operation
00	Pass the 1 st operand ($Y = A$)
01	Pass the 2 nd operand ($Y = B$)
10	Add the 2 operands ($Y = A+B$)
11	Bit-wise AND the 2 operands ($Y = A \text{ AND } B$)

The ALU unit takes **2 4-bits input** (A, B) and **1 4-bits output** (Y), as shown in figure 1. The ALU also takes **1 2-bit selector** (S) to choose the required operations. Make any extra assumptions you need.

Requirements:

- 1- Create a schematic file and implement the ALU operation
- 2- Create another schematic file and use the ALU as a component (check slide 31 & 32 in the lab)
- 3- Create a waveform file and set a test scenario
- 4- Compile and simulate your design

Deadline:

You will need it in your next assignment, so please